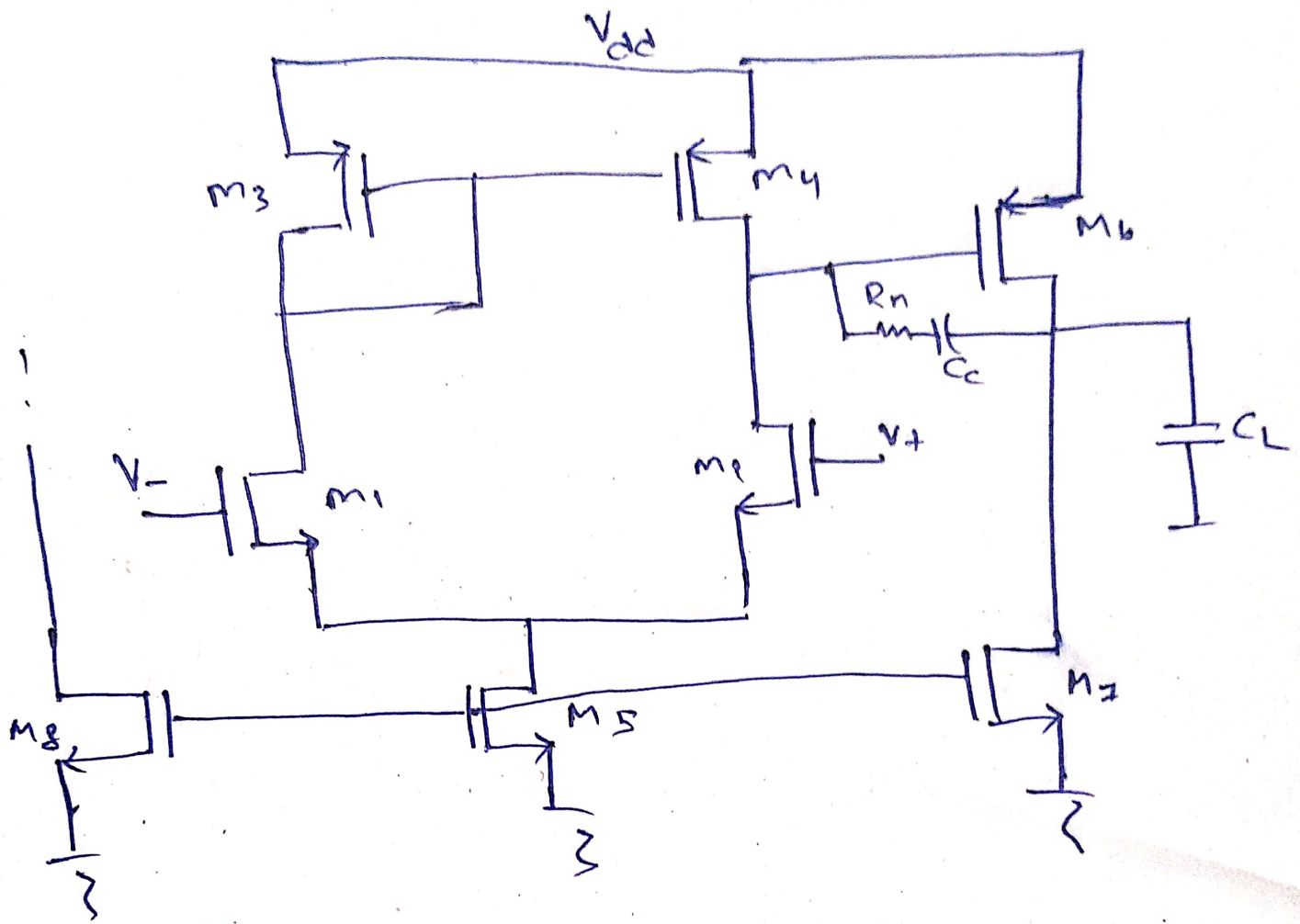


Two-stage - opamp -



Design constraints,

$$C_L = 5\text{pF}$$

$$\text{Power consumption} = < 0.5\text{mW}$$

$$\text{Unity Gain BW} = > 10\text{MHz}$$

$$\text{Slew rate} = 15\text{V}/\mu\text{s}$$

$$\text{Gain} > 90\text{dB}$$

$$\text{PM} > 75^\circ$$

For M_1 & M_2 :-

$$g_{m1} = 2\pi \times \text{GBW} \times C_c$$

$$= 2\pi \times 10 \times 2$$

$$g_{m1} = 125.6 \mu$$

$$\begin{cases} C_L = 5\text{pF} \\ C_c = 4C_L \\ C_c = 2\text{pF} \end{cases}$$

Consider
~~Given~~

$$\text{Slew rate} = 15 \text{ V}/\mu\text{s} \quad \left(\text{S.R} = \frac{I_o}{C_c} \right)$$

$$\begin{aligned} I_{\text{Tail}} &= 15 \times 2 \\ &= 30 \mu \end{aligned}$$

$$I_{\text{Tail}} = 30 \mu$$

$$\begin{aligned} \left(\frac{\omega}{L} \right)_1 &= \frac{g_{m1}^2}{\mu_n C_{ox} 2 I_{o1}} \\ &= \frac{(125.6)^2}{30 \times 2 \times 15} \\ &= 1.78 \mu \end{aligned}$$

$$\left(\frac{\omega}{L} \right)_{1/2} \approx 2 \mu$$

Using Miller Compensation: -

→ Let us assume that ^{due to} the zero which is created due to miller cap is 10 times bigger than GBP

$$Z_1 \geq 10 \text{ GBP}$$

$$PM = 180 - \tan^{-1}\left(\frac{GBP}{Z}\right) - \tan^{-1}\left(\frac{GBP}{P_1}\right) - \tan^{-1}\left(\frac{GBP}{P_2}\right)$$

→ Let us assume that gain of the op amp is very high such that $\tan^{-1}(A_{dc})$ can go up to 90° .

$$\therefore PM = 180 - 95.17 - \tan^{-1}\left(\frac{GBP}{P_2}\right)$$

We have considered, $PM = 70^\circ$

$$\therefore \tan^{-1} \frac{GBP}{P_2} = 14.29$$

$$\boxed{P_2 = 4 \text{ GBP}}$$

From this, $C_c = 0.4 C_L$

For M_b :-

we have assumed,

$$z_1 = 10 \text{ GBP}$$

$$\frac{g_{m_b}}{C_C} \geq 10 \frac{g_{m_1}}{C_C}$$

$$\boxed{g_{m_b} \geq 10 g_{m_1}}$$

$$\therefore g_{m_b} = 1250 \mu$$

But from the test circuit g_{m_1} was found to be, ~~117~~ 117μ

$$\therefore g_{m_1} = 117 \mu$$

$$\therefore g_{m_b} = 1170 \mu$$

$$\left(\frac{\omega}{L}\right)_b = \frac{g_{m_b}}{g_{m_u}} \left(\frac{\omega}{L}\right)_u$$

Also found from test circuit.

$$= \frac{1170}{208.9} \times 14.5$$

$$= 268.8$$

$$\left(\frac{\omega}{L}\right)_b \approx 269$$

now

$$I_b = \frac{269}{11.3} \times 15$$

$$I_b = \frac{\left(\frac{\omega}{L}\right)_b}{\left(\frac{\omega}{L}\right)_u} \times I_u$$

$$I_b = 98.41 \mu A$$

For M_7 :

$$\left(\frac{\omega}{L}\right)_7 = \frac{I_{70}}{I_5} \times \left(\frac{\omega}{L}\right)_{I_5}$$

$$= \frac{98.41}{30} (20)$$

$$\left(\frac{\omega}{L}\right)_7 = 65.60$$

→ To increase the PM & GBP, we are using nulling resistor such that it will compensate the non-dominant pole and increase the gap between P_1 & P_3 such that PM will increase.

$$R_N = \left(\frac{C_C + C_L}{C_C} \right) \frac{1}{g_{m6}}$$
$$= \left(\frac{2+5}{2} \right) \frac{1}{1170}$$

$$R_N = 2.99 \text{ K}$$

$$R_N \approx 3 \text{ K } \Omega$$

After adding Miller Cap & nulling Res:-

$$\omega_{P1} = \frac{1}{g_{m1} R_1 R_2 C_c} \quad , \quad \omega_{P2} = \frac{g_{m6}}{C_L}$$

$$\omega_{P3} = \frac{1}{R_2 C_1} \quad , \quad \omega_{Z1} = \frac{1}{C_c \left(\frac{1}{g_{m5}} + R_2 \right)}$$

$$\boxed{\omega_{Z1} = \omega_{P2}} = 1 \text{ For inc PM}$$

From this we get, R_1

Tuning the parameters:-

→ Since the square law method is approximate method and we don't get exact results.

→ Tuning the parameters is important to get expected results.

After tuning:

For $M_{1,2}$:-

$$\left(\frac{W}{L}\right) = 2,$$

$$W = 4 \mu m$$

$$L = 2 \mu m$$

For M_3, M_4 :-

$$\left(\frac{W}{L}\right) = 41$$

$$W = 20.5 \mu$$

$$L = 500 n$$

For M_5, M_6 :-

$$\left(\frac{W}{L}\right) = 20$$

$$W = 20 \mu$$

$$L = 1 \mu$$

For M_6 :-

$$\left(\frac{W}{L}\right) = 269$$

$$W = 134.5 \mu$$

$$L = 500 n$$

For M_7 :-

$$\left(\frac{W}{L}\right) = 65.6 \mu$$

$$W = 65.6 \mu$$

$$L = 1 \mu$$

For nulling resistor, $R_N = 2.89 k$ ohms after tuning.